



VIT[®]
Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

A

Project Report on

"Melodic Beats: Creating a Piano Circuit with IC 555 Timer"

Subject :Analog Circuits

Submitted to: Boopalan G

Slot :L47+L48,L33+L34


BY :

22BEC0538 Vamsi Krishna sigatapu

23BEC0142 KAUSHIK KUMAR PS

23BML0100 Adarsh V V

Schematic (Multisim):

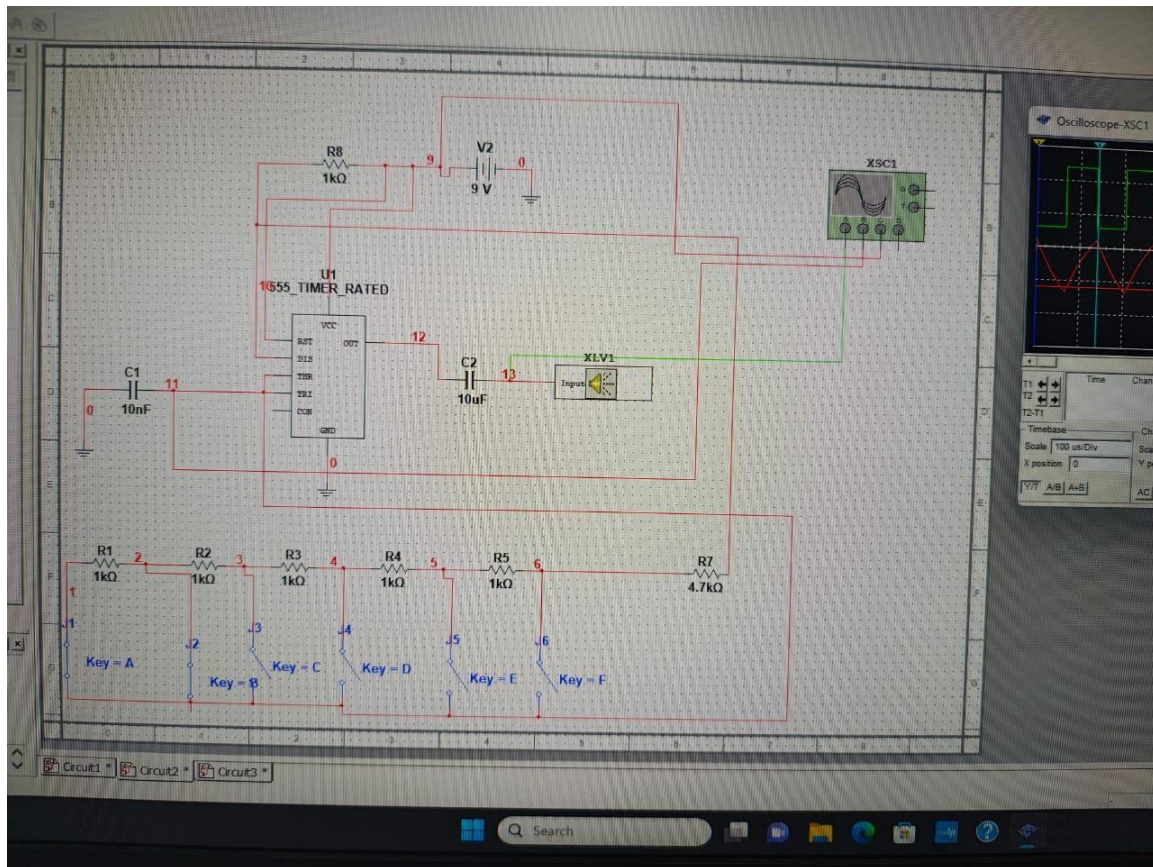

Simulation results :




Result:

Changing the resistor value in series with the capacitor changed the frequency of the circuit.
Increasing the resistance produce a lower sound, while decreasing the resistance made the LED blink faster or produced a higher sound.

Photos:



FABRICATION:

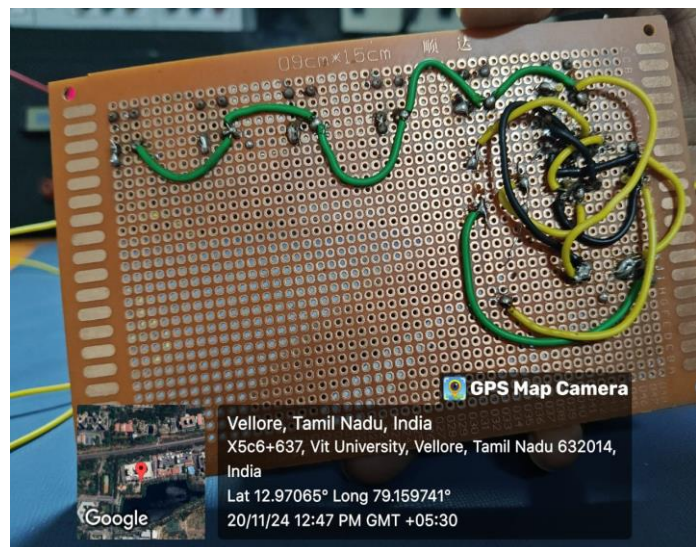

References:

1. <https://howtomechatronics.com/how-it-works/555-timer-ic-working-principle-block-diagram-circuit-schematics/>
2. <https://howtomechatronics.com/how-it-works/555-timer-ic-working-principle-block-diagram-circuit-schematics/>
3. <https://www.circuitbasics.com/555-timer-basics-astable-mode/>